

Exam 2

**P208 Fall 2009,
Instructor: Prof. Abanov**

10/12/09

Name _____
(print)


Section _____

501 Fuller, Melissa	Tues, 2:20-5:10	516 Li, Feng	Thurs, 8:00-10:50
502 Mahony, James	Tues, 3:55-6:45	517 Amin, Vivek	Thurs, 9:35-12:25
503 Chen, Jason	Tues, 4:55-7:45	518 Chen, Jason	Thurs, 11:10-2:00
504 Ferguson, Jim	Tues, 5:55-8:45	519 Russell, Charles	Thurs, 12:45-3:35
505 Zhang, Xiwen	Tues, 6:55-9:55	520 Zhang, Xiwen	Thurs, 2:20-5:10

Your grade:

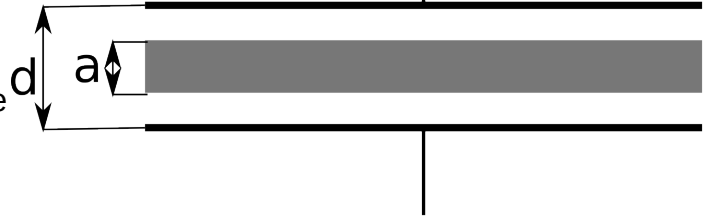Problem 1.

A parallel plate air capacitor is made using square L by L plates. The distance between the plates is d . A metal slab having thickness a ($a < d$) and the same shape as the plates is inserted in the middle between the plates as shown on the figure.



What is the capacitance of this capacitor without the slab? _____

What is the capacitance of this arrangement with the slab? _____


How will the capacitance change if we move the slab up or down (without touching the plates)? _____

How will the capacitance change if we move the slab a distance x to the right?

Or to the left? _____

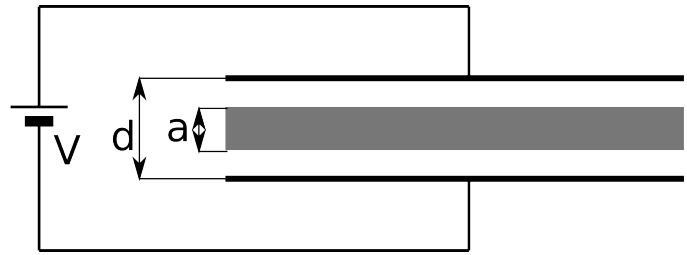Problem 2.

A parallel plate air capacitor is made using square L by L plates. The distance between the plates is d . A metal slab having thickness a ($a < d$) and the same shape as the plates is inserted in the middle between the plates as shown on the figure.



The capacitor is connected to the battery with emf V .

What is the charge on the capacitor without the slab? _____

What is the charge on the plates when the slab is inserted? _____

What will the charge on the plates be if you move the slab the distance x to the right? _____

What is the total work done by the battery after you have moved the slab? _____


What is the change of the energy stored in the capacitor? _____

What is the total work done by YOU after you have moved the slab?

What is the minimal force you have to apply to the slab in order move it?

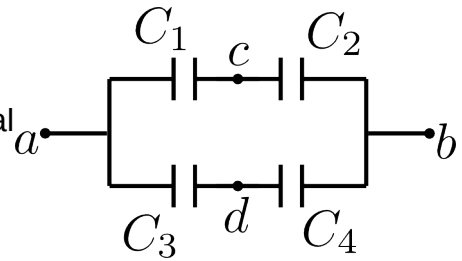Problem 3.

In the figure $C_1=C_4=6\mu F$ and $C_2=C_3=3\mu F$. The potential difference between points a and b is kept $V_{ab}=3V$ by a battery.



What is the charge on each capacitor? C_1 _____, C_2 _____,
 C_3 _____, C_4 _____,

What is the potential difference between points a and c , V_{ac} ?

What is the potential difference between points a and d , V_{ad} ?

What is the potential difference between points c and d , V_{cd} ?

Problem 4.

A current $I=1.6\text{A}$ is in a copper wire (resistivity $\rho=1.7\times 10^{-8}\Omega\cdot\text{m}$) with cross section area $A=5.88\times 10^{-7}\text{m}^2$ and length $L=100\text{m}$.

What is the resistance of the wire?_____

How many electrons are crossing a cross section of the wire each second?_____

What is the current density in the wire?_____

What is the magnitude of the electric field in the wire?_____

What is the potential difference between the ends of the wire?_____

Problem 5.

A battery with $E=12V$ and internal resistance $r=3k\Omega$ is connected to a simple circuit with a total resistance of $R=9k\Omega$.

What is the current through the battery?_____

What is the potential difference between the battery's terminals?_____

How much power does the battery supply to the simple circuit?_____

How much power dissipates inside the battery?_____

Problem 6.


You have a meter with resistance $30\ \Omega$ and full-scale current $I_{fs}=1\text{mA}$.

Design an ammeter with a range 0 to 50mA (draw schematics and calculate the resistance of the shunt resistor).

What is the total resistance of your ammeter?_____

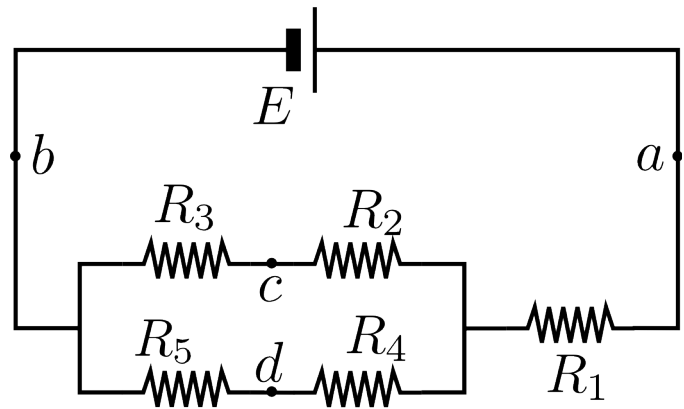Problem 7.

In the circuit shown in the picture
 $E=12V$, $R_1=2k\Omega$, $R_2=1k\Omega$,
 $R_3=2k\Omega$, $R_4=2k\Omega$, $R_5=4k\Omega$.



What is the potential difference between points a and b ? _____

What is the current at point a of the circuit? _____


What is the the current at point c ? _____

What is the the current at point d ? _____

What is the potential difference between points c and d ? _____

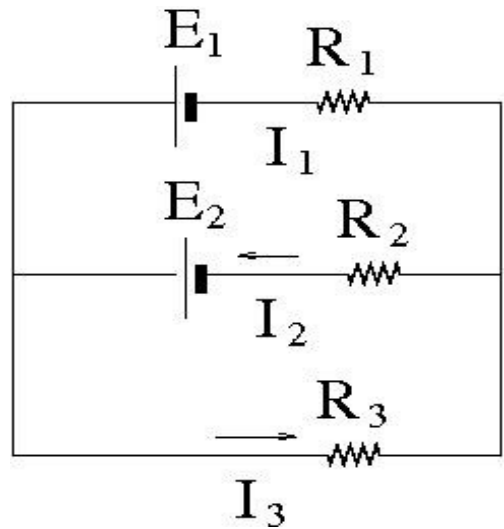Problem 8.

In the circuit shown in the figure $R_1=1k\Omega$,
 $R_2=4k\Omega$, $R_3=3k\Omega$, $I_2=4mA$, and $I_3=6mA$
(directions of I_2 and I_3 are shown)




What is the magnitude and direction (show in the figure) of the current I_1 ? _____

What is the value of the emf E_1 ? _____

What is E_2 ? _____

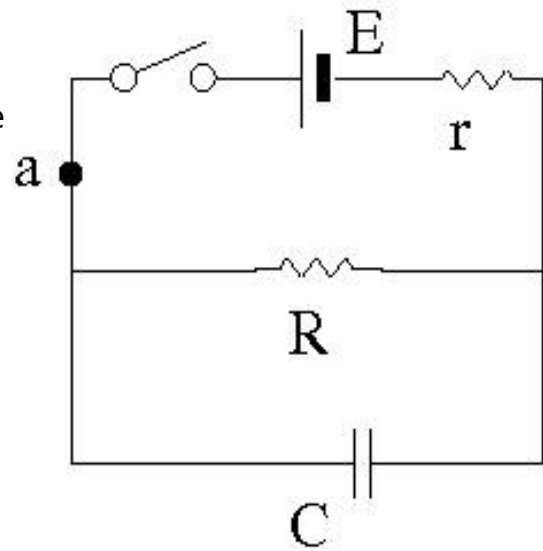Problem 9.

In the circuit shown in the figure $E=12V$,
 $r=2k\Omega$, $R=4k\Omega$, and $C=4\mu F$. Initially the
capacitor is uncharged. The switch is closed at
moment t_0 .




What is the current in point "a" immediately after t_0 ? _____

What is the current in point "a" after a very long time? _____

What is the charge on the capacitor C long after time t_0 ? _____

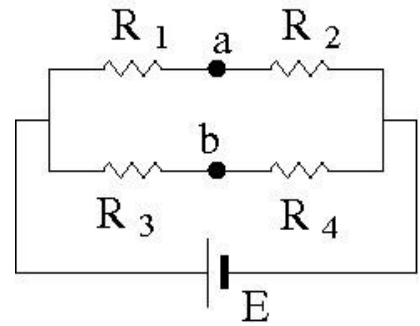Problem 10.

In the circuit shown on the figure $R_1=3\text{k}\Omega$, $R_2=9\text{k}\Omega$, and $R_3=5\text{k}\Omega$.



What is the necessary value of R_4 such that the potential difference between points a and b is 0 ? _____


For R_4 which you calculated before what will be the current through a $12\text{k}\Omega$ resistor placed between the points a and b ? _____

Extra Problems.

Please take this page with you. You have all the time till the final exam to solve these problems. The first student who solves one of the problems will get 5 bonus points for this exam.

Extra Problem 1.

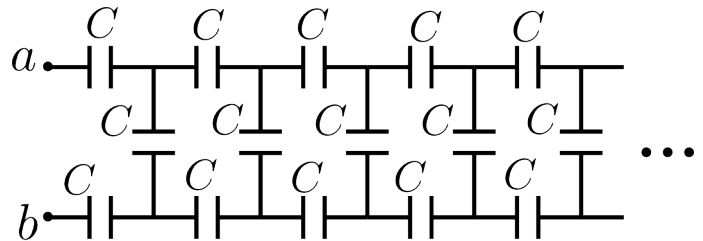The capacitance of each capacitor of the **infinite** series shown in the picture is $C=1\mu F$. Find the total capacitance between points a and b .



Extra Problem 2.

An **infinite** square lattice is made of identical capacitors of capacitance $C=1\mu F$.

Find the capacitance between nearest neighbor vertices a and b .

