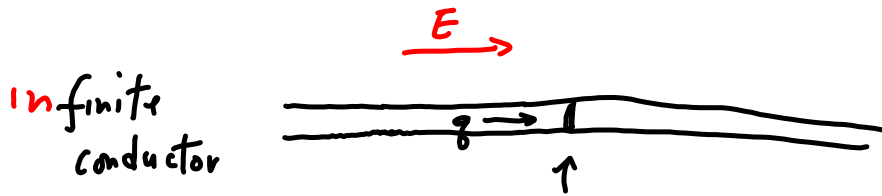


Electric Charge  $\rightarrow$  Electric field  $\rightarrow$  Electric flux

$\rightarrow$  Electric potential  $\rightarrow$  Electric flow  $\rightarrow$  Electric circuit.



electric current  $I = \frac{\Delta q}{\Delta t} = \frac{\text{amount of charge}}{\text{unit time}}$

const  $I \Rightarrow$  const velocity flow

for a const  $E \Rightarrow F = qE$

const  $E \rightarrow$  const acceleration  $\Rightarrow a = \frac{qE}{m}$   $ma = qE$

$v = at = \frac{qE}{m} t$


for  $t = \tau$

$v = v_d = \frac{qE}{m} \tau$

under  $\vec{E}$  + collision  $\Rightarrow$  const velocity flow  $\Rightarrow I$

potential  $V \rightarrow$  current flow

However, with  $E \rightarrow$

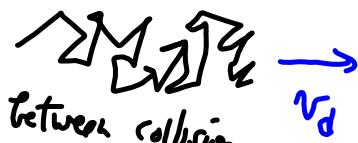

average time between collision


for Given  $V$ , cause a current  $I$  of

Current  $\rightarrow I = \frac{V}{R}$   $\leftarrow$  pot diff or voltage  $\leftarrow$  resistance of the material  $\leftarrow$  Ohm's Law.

$[a = \frac{F}{m}]$

Current flows in direct proportion to the applied voltage + inversely proportional to the resistance.

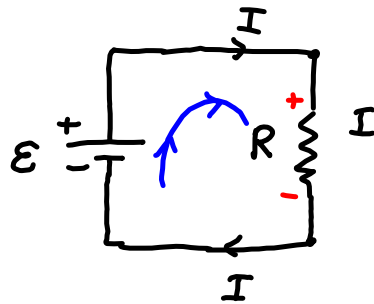Current flow is maintained by a "potential pump"




$$\Delta V_{\epsilon} + \Delta V_R = 0$$

$$\epsilon - V = 0$$

$$\epsilon = IR \Rightarrow I = \frac{\epsilon}{R}$$

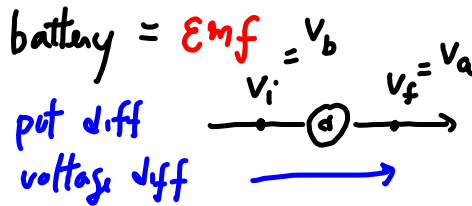
- 1) + sign where the current enters the device
- sign where it exits



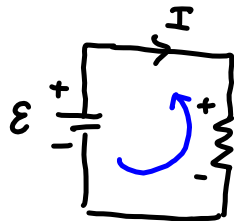2) Kirchhoff Rule:

The sum of all pot. diff. across all devices must be zero.

choose a direction of calculation:  $\Delta V = V_{after} - V_{before}$



$$\Delta \epsilon + \Delta R = 0$$

$$-\epsilon + IR = 0$$

$$I = \frac{\epsilon}{R} !$$

## Power dissipation in a resistor

$$P = \frac{\Delta W}{\Delta t} = \frac{\text{work done}}{\text{unit time}} = \frac{\Delta U}{\Delta t} = \frac{qV}{\Delta t} = IV$$

↙ pot.

$$P = IV$$

since



$$V = IR$$

$$\rightarrow I = \frac{V}{R}$$


either  
current

$$= I^2 R$$

$$= \frac{V^2}{R}$$

or  
the voltage

Apply Kirchoff's rule

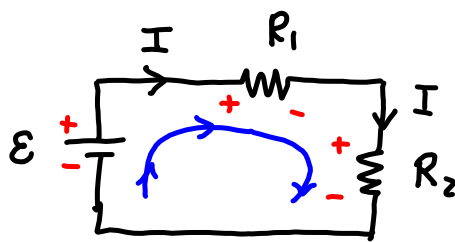

$$\Delta V_{\epsilon} + \Delta V_{R_1} + \Delta V_{R_2} = 0$$

$$\epsilon - IR_1 - IR_2 = 0$$


$$\epsilon = I(R_1 + R_2)$$

$$I = \frac{\epsilon}{R_1 + R_2} \stackrel{\text{def}}{=} I_{\text{eff}}$$

Resistors in series:

$$R_{\text{eff}} = R_1 + R_2 + R_3$$

Same  
current

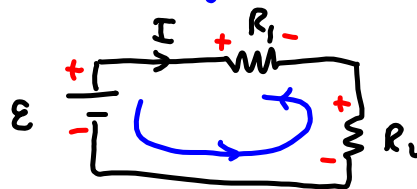


$$\Delta V_{\epsilon} + \Delta V_{R_1} + \Delta V_{R_2} = 0$$

$$-\epsilon + IR_2 + IR_1 = 0$$

$$I = \frac{\epsilon}{R_1 + R_2}$$

Ex 3:

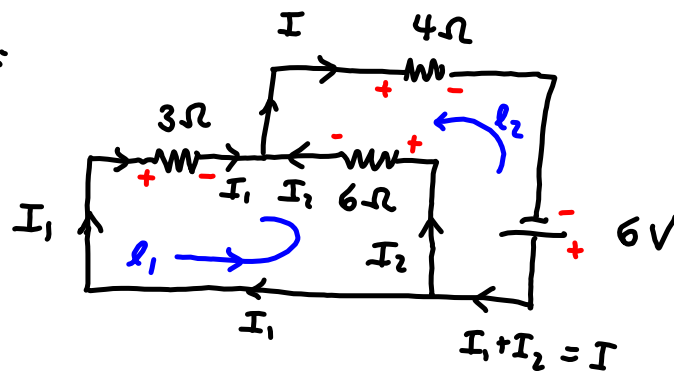Find all  
currents  
flowing  
thru each  
device



$$l_1: \Delta V_6 + \Delta V_3 = 0$$

$$-I_2 6 + I_1 3 = 0$$

$$3I_1 = 6I_2$$

$$I_1 = 2I_2$$

$$I_2 = \frac{6}{18} = \frac{1}{3}$$

$$l_2: -6 + 4(I_1 + I_2) + 6I_2 = 0$$

$$6I_2 + 4I_1 + 4I_2 = 6$$


$$10I_2 + 4I_1 = 6$$

$$10I_2 + 4(2I_2) = 6$$

$$18I_2 = 6$$

Ex 4 : Two batteries

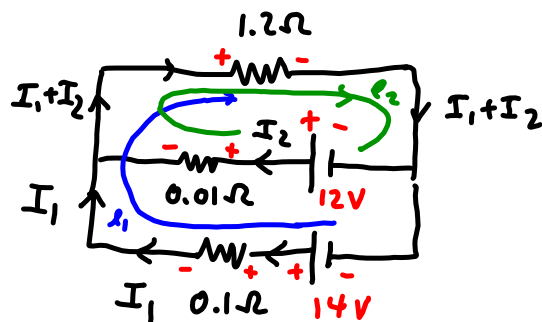Find all  
current  
thru  
each  
resistor



$$l_1: 14 - I_1 \cdot 0.1 - (I_1 + I_2) \cdot 1.2 = 0$$

$$l_2: 12 - I_2 \cdot 0.01 - (I_1 + I_2) \cdot 1.2 = 0$$

$$14 = 1.3 I_1 + 1.2 I_2$$

$$12 = 1.21 I_2 + I_1 \cdot 1.2$$

↑

$$I_2 = \frac{12 - I_1 \cdot 1.2}{1.21}$$


$$14 = 1.3 I_1 + 1.2 \left( \frac{12 - I_1 \cdot 1.2}{1.21} \right)$$

$$= 1.3 I_1 + \frac{1.2 \cdot 12}{1.21} - I_1 \frac{(1.2)^2}{1.21}$$

$$I_1 = 19.1 \text{ A}$$

$$I_2 = -9.02 \text{ A}$$

Ex.

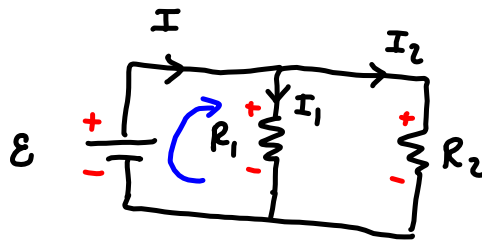

$$I = I_1 + I_2$$

→  
in parallel  
having the  
same voltage

$$\Delta V_{\epsilon} + \Delta V_{R_1} = 0$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\epsilon - I_1 R_1 = 0$$

$$\epsilon - I_2 R_2 = 0$$

$$\Rightarrow I_1 = \frac{\epsilon}{R_1}$$

$$I_2 = \frac{\epsilon}{R_2}$$

$$I = \frac{\epsilon}{R_1} + \frac{\epsilon}{R_2} = \epsilon \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \epsilon \frac{1}{R_{eq}}$$