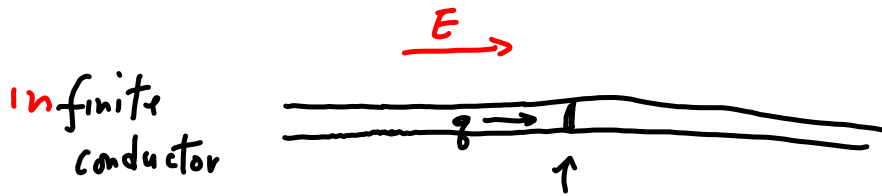


Electric Charge \rightarrow Electric field \rightarrow Electric flux
 \rightarrow Electric potential \rightarrow Electric flow \rightarrow Electric circuit.



electric current $I = \frac{\Delta q}{\Delta t} = \frac{\text{amount of charge}}{\text{unit time}}$

const $I \Rightarrow$ const velocity flow

for a const $E \Rightarrow F = qE$


const $E \rightarrow \Rightarrow a = \frac{qE}{m}$ $ma = qE$
 const acceleration

$v = at = \frac{qE}{m} t$

for $t = \tau$

$v = v_d = \frac{qE}{m} \tau$

However, with $E \rightarrow$

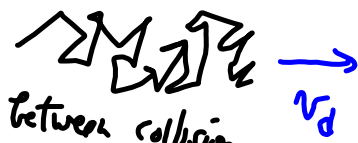

under \vec{E} + collision \Rightarrow const velocity flow $\Rightarrow I$

potential $V \rightarrow$ current flow


for Given V , cause a current I of

Current $\rightarrow I = \frac{V}{R}$ \leftarrow pot diff or voltage
 \leftarrow resistance of the material
 \leftarrow Ohm's Law.

$[a = \frac{F}{m}]$

Current flows in direct proportion to the applied voltage + inversely proportional to the resistance.

More details on Ohm's Law:

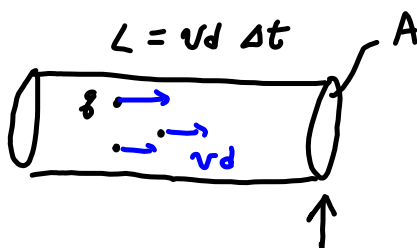

Let $\eta = \frac{\text{\# of charges}}{\text{Volume}}$
 = charge density

find current $I = \frac{\Delta q}{\Delta t} = \frac{q \text{ Vol} \cdot \eta}{\Delta t} = \frac{(A v_d \cancel{\Delta t}) \eta q}{\cancel{\Delta t}}$

$$I = A v_d \eta q$$

$$V = E d$$

$$= E L$$

$$= A \frac{q E \tau \eta q}{m}$$

$$I = \frac{A q}{m} \frac{V}{L} \tau \eta q = \frac{A V}{L} \frac{q^2 \tau \eta}{m}$$

$$= \frac{A q}{m} \eta \frac{V}{L} = \frac{A}{L} \frac{V}{\rho}$$

$$\rho = \frac{m}{q^2 \tau \eta}$$


$$I = \frac{A}{L \rho} V = \frac{V}{R}$$

Ohm's Law

resistivity of the material

$$R = \frac{L \rho}{A}$$

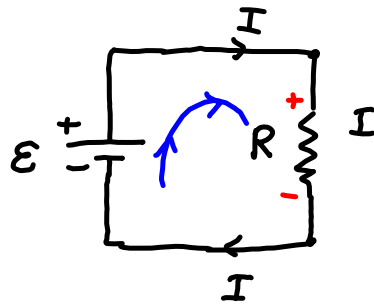Current flow is maintained by a "potential pump"




$$\Delta V_{\epsilon} + \Delta V_R = 0$$

$$\epsilon - V = 0$$

$$\epsilon = IR \Rightarrow I = \frac{\epsilon}{R}$$

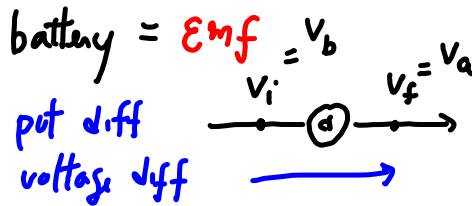
- 1) + sign where the current enters the device
- sign where it exits



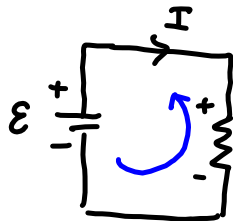2) Kirchhoff Rule:

The sum of all pot. diff. across all devices must be zero.

choose a direction of calculation: $\Delta V = V_{after} - V_{before}$



$$\Delta \epsilon + \Delta R = 0$$

$$-\epsilon + IR = 0$$

$$I = \frac{\epsilon}{R} !$$

Power dissipation in a resistor

$$P = \frac{\Delta W}{\Delta t} = \frac{\text{work done}}{\text{unit time}} = \frac{\Delta U}{\Delta t} = \frac{qV}{\Delta t} = IV$$

↙ pot.

$$P = IV$$

since



$$V = IR$$

$$\rightarrow I = \frac{V}{R}$$


either
current

$$= I^2 R$$

$$= \frac{V^2}{R}$$

or
the voltage

Apply Kirchoff's rule

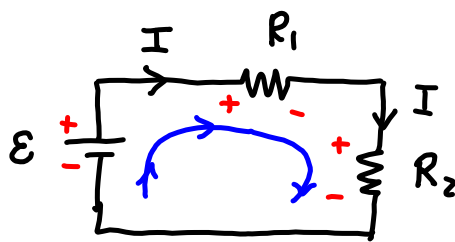

$$\Delta V_{\epsilon} + \Delta V_{R_1} + \Delta V_{R_2} = 0$$

$$\epsilon - IR_1 - IR_2 = 0$$


$$\epsilon = I(R_1 + R_2)$$

$$I = \frac{\epsilon}{R_1 + R_2} \stackrel{\text{def}}{=} I_{\text{eff}}$$

Resistors in series:

$$R_{\text{eff}} = R_1 + R_2 + R_3$$

Same
current

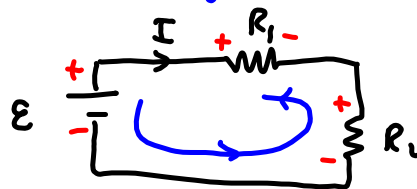


$$\Delta V_{\epsilon} + \Delta V_{R_1} + \Delta V_{R_2} = 0$$

$$-\epsilon + IR_2 + IR_1 = 0$$

$$I = \frac{\epsilon}{R_1 + R_2}$$

Ex 3:

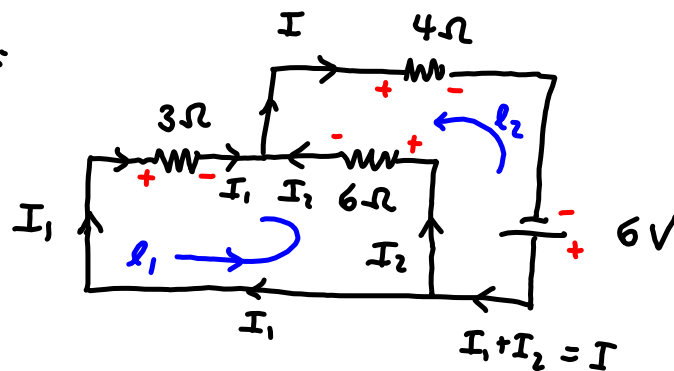Find all
currents
flowing
thru each
device



$$l_1: \Delta V_6 + \Delta V_3 = 0$$

$$-I_2 6 + I_1 3 = 0$$

$$3I_1 = 6I_2$$

$$I_1 = 2I_2$$

$$I_2 = \frac{6}{18} = \frac{1}{3}$$

$$l_2: -6 + 4(I_1 + I_2) + 6I_2 = 0$$

$$6I_2 + 4I_1 + 4I_2 = 6$$


$$10I_2 + 4I_1 = 6$$

$$10I_2 + 4(2I_2) = 6$$

$$18I_2 = 6$$

Ex 4 : Two batteries

Find all
current
thru
each
resistor

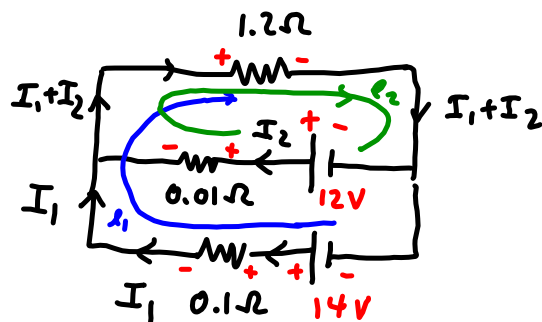

$$l_1: 14 - I_1 \cdot 0.1 - (I_1 + I_2) \cdot 1.2 = 0$$

$$l_2: 12 - I_2 \cdot 0.01 - (I_1 + I_2) \cdot 1.2 = 0$$

$$14 = 1.3 I_1 + 1.2 I_2$$

$$12 = 1.21 I_2 + I_1 \cdot 1.2$$

↑

$$I_2 = \frac{12 - I_1 \cdot 1.2}{1.21}$$


$$14 = 1.3 I_1 + 1.2 \left(\frac{12 - I_1 \cdot 1.2}{1.21} \right)$$

$$= 1.3 I_1 + \frac{1.2 \cdot 12}{1.21} - I_1 \frac{(1.2)^2}{1.21}$$

$$I_1 = 19.1 \text{ A}$$

$$I_2 = -9.02 \text{ A}$$

Ex.

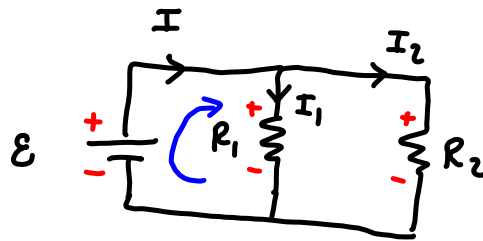

$$I = I_1 + I_2$$

→
in parallel
having the
same voltage

$$\Delta V_{\epsilon} + \Delta V_{R_1} = 0$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\epsilon - I_1 R_1 = 0$$


$$\epsilon - I_2 R_2 = 0$$

$$\Rightarrow I_1 = \frac{\epsilon}{R_1}$$

$$I_2 = \frac{\epsilon}{R_2}$$

$$I = \frac{\epsilon}{R_1} + \frac{\epsilon}{R_2} = \epsilon \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \epsilon \frac{1}{R_{eq}}$$

Discharging the capacitor

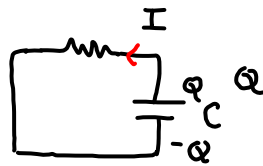

$$IR + \frac{q}{C} = 0 \quad \text{in time } \Delta t$$

$$\frac{\Delta q}{\Delta t} R + \frac{q}{C} = 0 \Rightarrow \Delta q = -\frac{q}{RC} \Delta t$$

$$\text{in time } \Delta t : q(\Delta t) = q_0 + \Delta q \quad \leftarrow \text{initial charge} = Q$$

$$q(\Delta t) = q_0 - \frac{q_0 \Delta t}{RC} = q_0 \left(1 - \frac{\Delta t}{RC}\right)$$

$$q(2\Delta t) = q(\Delta t) \left(1 - \frac{\Delta t}{RC}\right) = q_0 \left(1 - \frac{\Delta t}{RC}\right)^2$$

$$q(3\Delta t) = q(2\Delta t) \left(1 - \frac{\Delta t}{RC}\right) = q_0 \left(1 - \frac{\Delta t}{RC}\right)^3$$

$$t = n \Delta t$$

$$q(t) = q_0 \left(1 - \frac{\Delta t}{RC}\right)^n = q_0 \left(1 - \frac{t}{nRC}\right)^n$$

binomial expansion

$$\begin{aligned} \left(1 - \frac{t}{nRC}\right)^n &= 1 - \frac{t}{nRC} + \frac{n(n-1)}{2!} \left(\frac{t}{nRC}\right)^2 - \frac{n(n-1)(n-2)}{3!} \left(\frac{t}{nRC}\right)^3 + \dots \\ &= 1 + nx + \frac{n(n-1)}{2!} x^2 + \dots \quad (1+x)^n \\ &= e^{-t/RC} \quad e = 2.71 \dots \end{aligned}$$


$$q(t) = q_0 e^{-t/RC}$$

$$= \frac{q_0}{e} \quad \text{if } t = t_0 \quad \underline{RC = t_0 = \text{characteristic time}}$$

$$q(t) = q_0 / e^2$$

$$t = 2t_0$$


$$t = 3t_0 \quad q(t) = q_0 / e^3$$

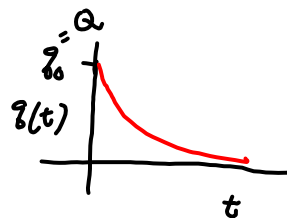


charging up the capacitor :

$$q(t) = Q \left(1 - e^{-t/RC}\right)$$


final charge

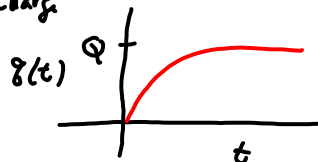

Ex. 1

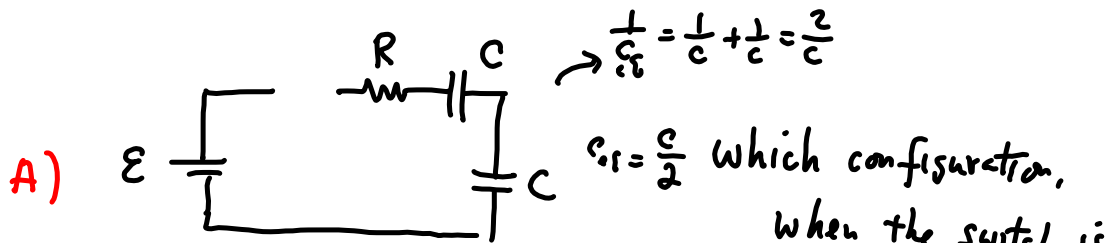

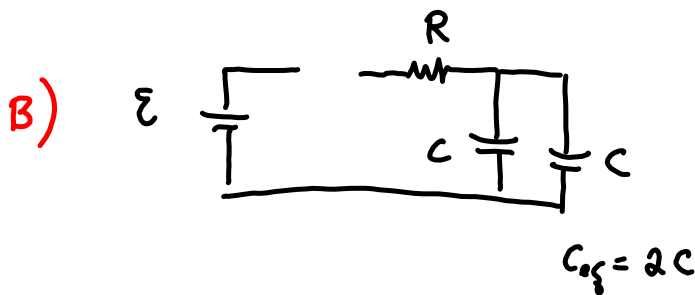Which configuration, when the switch is closed,




charges up the capacitors the **fastest**?

Review Chap 17-19


17) Coulomb force : for 3 charges

Electric field : $\vec{F} = q\vec{E}$

pt charge, charge plate, spherical shell

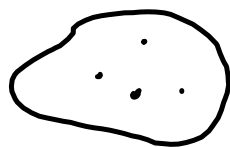Gauss' Law : electric flux $\Phi = AE$ 
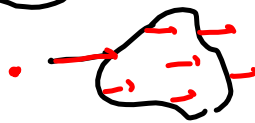
$$\Phi = 4\pi R^2 q_{enclosed} = \epsilon_0 q_{enclosed}$$



$$\Phi = 0$$



18) Electric potential

$$U = qV$$

↑ potential energy
↑ electric potential
 produced by pt charge,

a) V decreases in the direction of E .

Equipotential surfaces,

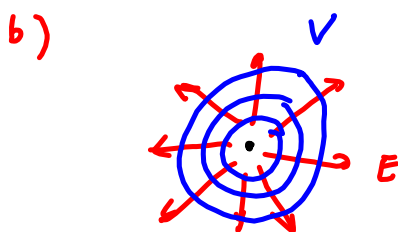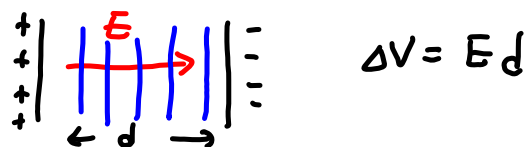

$$V = k \frac{q}{r}$$

c) Capacitor $Q = CV$ $U = \frac{1}{2} QV$
energy in a capacitor

Simple capacitance circuit. $U = Vu$ $u = \frac{1}{2} \epsilon_0 E^2$

dielectric $E = E_0 / K$ $C = K C_0$
↑ vacuum

19) Currents + Circuits

$$I = \frac{\Delta Q}{\Delta t}$$

$$V = IR$$

$$P = IV$$

↑
voltage across
the resistor

↖ power
dissipate in a resistor

Apply Kirchhoff's Rule to solve any two-loop
circuit



Sum of voltage difference
= 0

RC time scales, charging + discharging
a capacitor.